



Worcester Polytechnic Institute
Electrical and Computer Engineering Department

Methodologies for System Level Design and Modeling - ECE 5723

Online Offering – Fall 2020

Homework 1: Logic design, VHDL modeling, and testbench

Due Date: September 13

Description:

1. Write RT-level VHDL description for an 8-bit up counter with rising-edge clock, asynchronous reset, count-enable, load-enable, carry-in, carry-out, 8-bit parallel input, and 8-bit parallel output. All control inputs are active high.
2. Use a Toggle Flip-Flop (T-FF) and the counter in Part 1 to build a circuit that divides the clock frequency by 462 with a 50 percent duty cycle. For dividing the clock frequency (cf) by number d (here d is 462), you are to use a modulo- n counter (here n is 256) that starts counting from $n-(d/2)$ and goes up to $n-1$. In this case, the frequency of the carry-out signal becomes $cf/(d/2)$. To achieve this, take the carry-out and run it into the counter load input. For the parallel input use $n-(d/2)$. When the count reaches $n-1$, carry-out becomes 1 that causes $n-(d/2)$ to be loaded into the counter on the next clock. Then the count continues until the count reaches $n-1$ again. In the next step, you should add a T-FF to the carry-out signal of the counter to produce the frequency cf/d with a 50 percent duty cycle. As you know, T-FF behaves as a “divide-by-2” counter.

When the counter first starts, it starts with 0. The first time around, divide by d will not happen and the counter counts n . You do not have to worry about this case, but you will get a bonus if you provide an initialization signal to take care of this situation.

- A. Show the schematic diagram of the frequency divider.
- B. Write the VHDL description of the frequency divider.
- C. Write a testbench for the circuit in VHDL that tests the correctness of your circuit.
- D. Show the results of the simulation including the counter clock, the carry-out signal, and the generated clock frequency (the output of the T-FF) in your report.

Attention:

This homework covers “Topic 0.1 - Logic review” and “Topic 0.2 - HDL Background” modules on Canvas.

Deliverables:

All your VHDL codes and a complete report containing all parts of the assignment. Make sure that your deliverable follows all mentioned rules in the assignment part of the "*ECE5723 - Comprehensive Syllabus 2020.pdf*" file. The file has been posted on Canvas.
