



Worcester Polytechnic Institute
Electrical and Computer Engineering Department

Methodologies for System Level Design and Modeling - ECE 5723

Online Offering – Fall 2020


Homework 4: SystemC RTL design

Due Date: October 18

Description:

You have already done C++ modeling of the average calculator circuit that produces the average of its serial 8-bit data received on its input. The circuit starts its operation with a complete pulse on *start* (0-1-0). After that, the next eight bytes on *data* will be received and the average of the eight will be calculated. When this is completed, the *avg* output will contain the integer part of the calculated average, and the *ready* signal becomes 1. This signal remains active until the next time that *start* becomes 1. Implementation of division by 8 can be performed by dropping three least significant bits.

 In this homework, you are to model the circuit using SystemC in two ways (Parts A, B and Part D). You can use the design provided for the Homework 2 solution.



- A. Show the schematic diagram of the datapath of this circuit and then implement the datapath (DP) of the circuit using SystemC RTL components.
- B. Show the controller state diagram of the circuit and then develop the controller unit (CU) using **Huffman model**.
- C. Complete the design of the average calculator circuit by wiring CU and DP in a top-level module and write a testbench to verify your design using four different scenarios.
- D. Develop a **cycle-accurate behavioral model (BFM: Bus Functional Model)** for the circuit and test it with the same scenarios as in Part C.

Attention:

This homework covers “Topic 4 - SystemC RTL Modeling” module on Canvas.

Deliverables:

All your SystemC codes and a complete report containing all parts of the assignment. Make sure that your deliverable follows all mentioned rules in the assignment part of the "*ECE5723 - Comprehensive Syllabus 2020.pdf*" file. The file has been posted on Canvas.
