



Worcester Polytechnic Institute
Electrical and Computer Engineering Department

Methodologies for System Level Design and Modeling - ECE 5723


Online Offering – Fall 2020

Homework 3: C++ RT-level design and modeling

Due Date: October 04

Description:

You are to design a circuit that counts the number of transitions that occur on its serial input. The circuit is a clocked circuit with a serial input, J . There is a *start* pulse and an *end* pulse. After the *start* pulse (0-1-0, guaranteed one pulse), the counting begins and continues until a pulse is detected on *end*. During this time, clocked-synchronous transitions are detected and counted on the J input. An 8-bit counter is used here and counting beyond 256 rolls over back to 0. Provide an asynchronous reset.

 

- A. Show the schematic diagram of the datapath of this circuit.
- B. Show the controller **state diagram** of the circuit.
- C. Develop the controller (CU) using C++ and the *bus* library discussed in class (Chapter 3). Use **Huffman model**.
- D. Implement the datapath (DP) of the circuit using *bus*-based components.
- E. Complete the design of the average calculator circuit by wiring CU and DP in a top-level module that properly orders the datapath and controller.
- F. Write a testbench and verify your design using four different scenarios.

Attention:

This homework covers “Topic 3 - RT level modeling with C++ procedural language” module on Canvas.

Deliverables:

All your C++ codes and a complete report containing all parts of the assignment. Make sure that your deliverable follows all mentioned rules in the assignment part of the "*ECE5723 - Comprehensive Syllabus 2020.pdf*" file. The file has been posted on Canvas.
